

Latch-Up Protection For MOSFET Drivers

Author: Microchip Technology Inc.

INTRODUCTION

Most CMOS ICs, given proper conditions, can “latch” (like an SCR), creating a short circuit from the positive supply voltage to ground. This application note explains how this occurs and what can be done to prevent it for MOSFET drivers.

CONSTRUCTION OF CMOS ICs

In fabricating CMOS ICs, parasitic bipolar transistors are formed as a by-product of the CMOS process (see Figure 1). These transistors are inherent in the CMOS structure and can't be eliminated. The P-channel device has a parasitic PNP and the N-channel has a parasitic NPN. Through internal connections, the two parasitics form a four-layer SCR structure (see Figure 1 and Figure 2).

The parasitic SCR can be turned on if the P+ of the N-channel drain is raised above V_{S+} . This action will bias the drain P+ of parasitic Q_1 (Q_1 's emitter), back through Q_1 's base and return to V_{S+} through bulk resistance R_1 . A similar situation can occur if the drain of the N-channel MOSFET (emitter of Q_2) is taken below the V_{S-} supply.

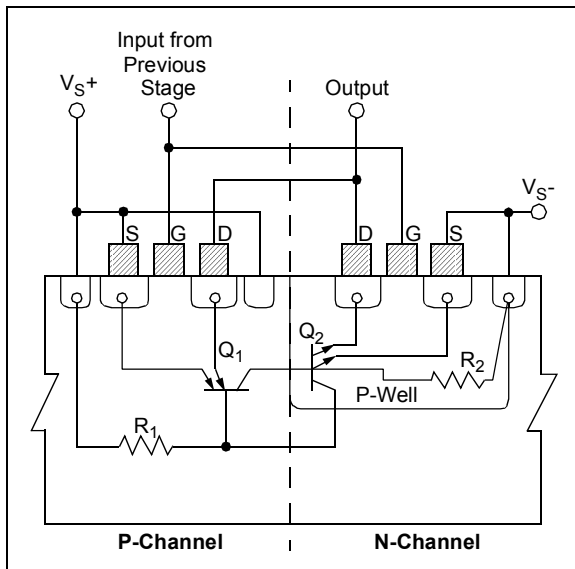


FIGURE 1: Output Stage IC Layout.

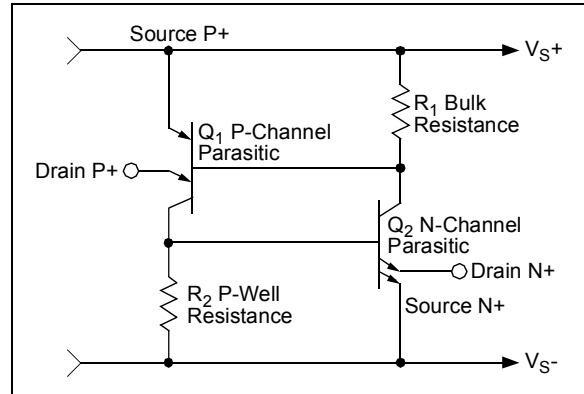


FIGURE 2: Equivalent SCR Circuit.

This emitter base junction of the parasitic bipolar is the parasitic diode that is also found in power MOSFETs. One of these diodes exists in every CMOS structure for both N- and P-channel devices. This corresponds with the fact that there exists a parasitic bipolar for every MOSFET in the IC, including the input transistors. Turn any one of them on and the SCR action will occur.

In most applications, the triggering of the parasitic SCR results in the destruction of the IC. The only time destruction does not occur is when the supply current to the device is limited. In this case, the device will resume normal operation when the parasitic SCR is unlatched by cycling the supply current through zero.

PREVENTING SCR TRIGGERING

Grounds

Clean grounds are important in any system, but they are especially important in analog and power processing circuits, becoming even more critical when CMOS ICs are used.

Poor ground practice can result in device latching. An example of this is shown in Figure 3. In this example, the PWM source sends the TC426 a “low” signal which causes the power MOSFET to turn “on”. If the ground return resistance (R_1) is sufficiently high, the ground voltage of the TC426 will rise above that of the PWM source, resulting in the input of the TC426 being negatively biased and will cause the TC426 to latch.

A similar condition can be caused by circuit inductance. Referring to Figure 3, assume R_1 is replaced by an inductor. When the MOSFET turns “on”, current in the source lead builds up very rapidly. Typical rise times would be about 30 nsec to 60 nsec.

AN763

For our example, assume that the MOSFET is switching 5A and the circuit inductance is 10 nH. From $V = L di/dt$, we can generate voltage shifts of 0.83V to 1.66V, depending upon the rise time, which is more than enough to trigger the parasitic SCR.

Troubleshooting this type of problem can be facilitated by placing a series resistor, typically 100Ω, between the TC426 and the MOSFET gate. This slows the MOSFET's transition and the circuit can be observed in operation without anything being destroyed. Be sure to take into account the increased dissipation in the MOSFET when using this technique.

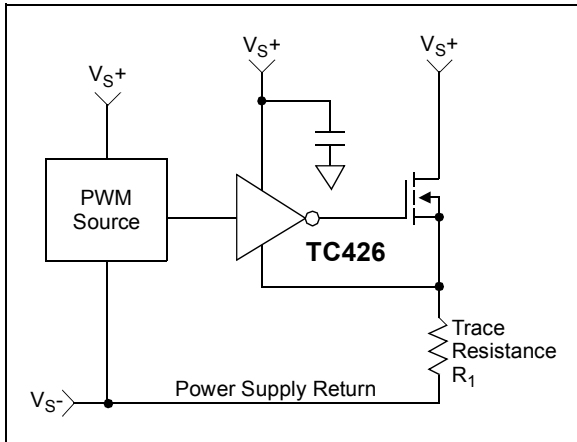


FIGURE 3: *Improper Ground.*

Figure 4 and Figure 6 show a proper “star” ground that will prevent latching. Notice all grounds meet only at one point. On a PC board, this means all traces must meet at one point, not that they are all connected to the same trace (Figure 3 and Figure 5 show this mistake).

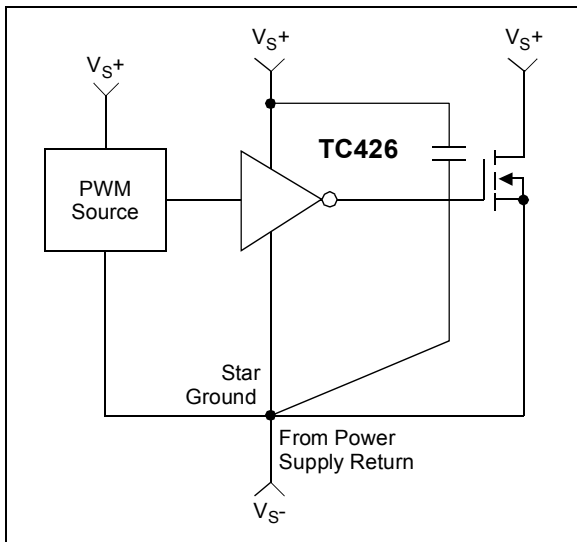


FIGURE 4: *Proper Ground.*

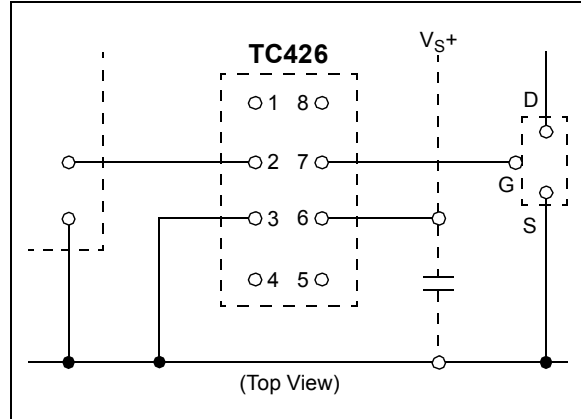


FIGURE 5: *Improper PC Layout.*

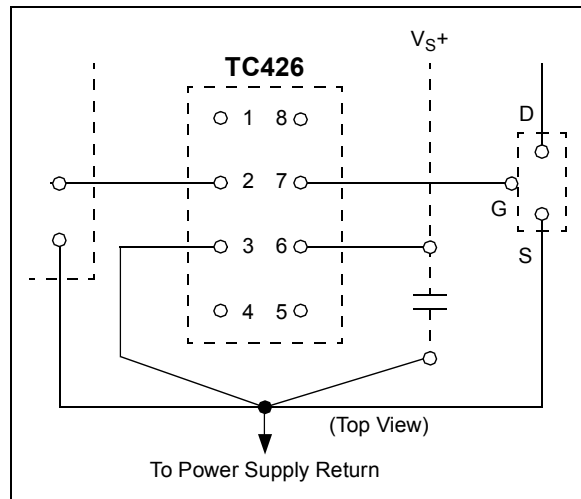


FIGURE 6: *Proper PC Layout.*

DECOUPLING

Ripple and noise on the power supply voltage is another source of latch-up problems. V_{S+} may be properly decoupled at the power supply, but at the supply pins of the IC, voltage transients occur. These transients are generated by the combination of the fast peak currents being drawn by the IC and the parasitic inductances and resistances of the power supply conductors (see Figure 7 and Figure 8).

This problem can be very pronounced with ICs driving large loads, as is the case of a TC426 or TC429 driving a power MOSFET. Upon switching, the TC429 can draw several amperes of current from the V_{S+} supply, causing large transients in the local supply voltage. If the TC429's input is very close to the system supply voltage, as it can be when being driven by CMOS logic, the local V_{S+} supply can drop significantly below the input, triggering the parasitic SCR. The parasitic SCR is very fast and this transition need last only a few nanoseconds for latching to occur.

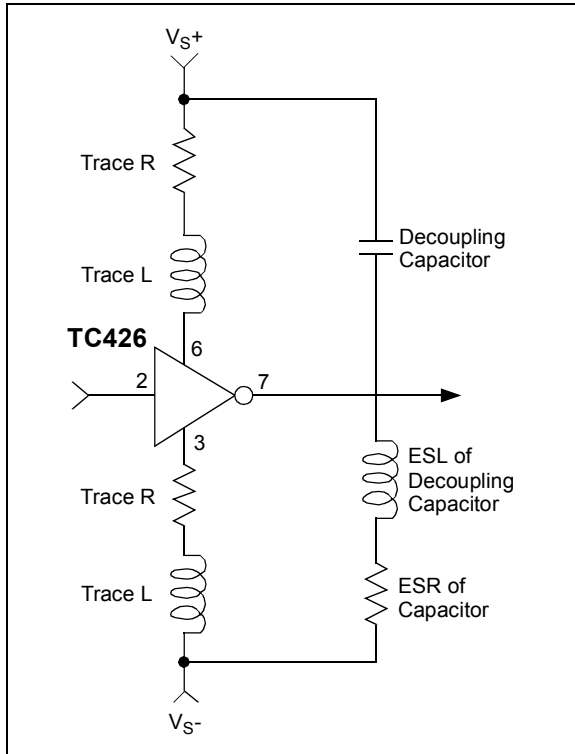


FIGURE 7: TC426 Fed by two PC Traces (Equivalent Circuit).

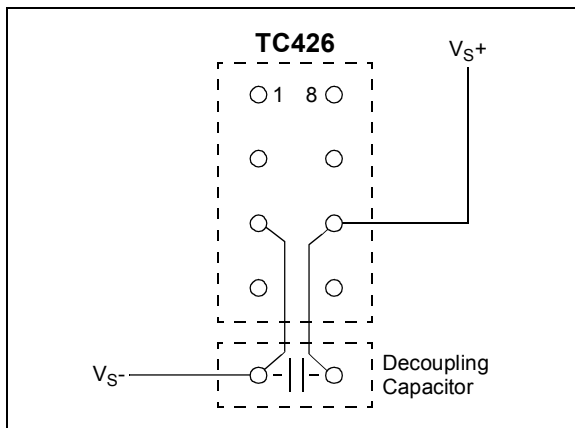


FIGURE 8: Typical PC Layout (TC426).

Aggravating this is the temperature dependence of the parasitic transistors. Their base emitter voltage decreases $\approx 2.2 \text{ mV}/^\circ\text{C}$ as temperature increases, making them increasingly more sensitive to transients as the chip temperature rises. Many times a system, which performed admirably on the bench, begins to experience problems at high temperatures because the local decoupling was marginal. The obvious solution is to properly decouple the supply bus so that V_{S+} can't drop below the value of the input signal. A second, less obvious, solution is to reduce the logic level applied to the input of the device.

Although lowering the input voltage will help the spikes that occur, they can cause other ICs on the same power supply to suffer noise immunity problems from the noise generated by the driver IC.

In some applications, such as portable instrumentation, it is desirable to keep the total power consumption at a minimum and designers will commonly shut off power to unused portions of the system to conserve battery life.

This can cause problems when an input signal is always present even though the V_{S+} line is turned "off". In this case, a resistor in series with the CMOS device's input will limit the injected current to a value below that listed in the device data sheet as "the maximum current into any pin". When V_{S+} is subsequently switched "on", the SCR action will be prevented.

DIODES

A very reliable method for preventing parasitic SCR action is to guard all the susceptible IC pins with steering diodes. This is most commonly done when a MOSFET driver is driving an inductive load, such as a long length of wire or a pulse transformer.

Placing a reverse-biased diode between each supply rail and the input/output pins (as shown in Figure 9 and Figure 10) limits the applied voltage swing to no more than the supply voltage plus the forward voltage drop of the clamping diode. For this reason, Schottky diodes are usually the best choice for this technique, as their forward voltage drop is less than the parasitic SCR's base emitter drop at any temperature. A Philips™/Mullard™/Amperex™ BYV10-30, for example, will work well for higher-power applications, such as MOSFET drivers. A BAT54 dual diode works well for surface-mount applications and with lower power ICs, such as operational amplifiers and A/D converters.

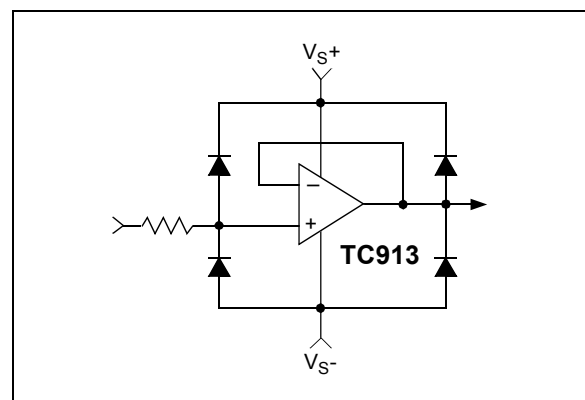


FIGURE 9: TC913 with Diode Clamps.

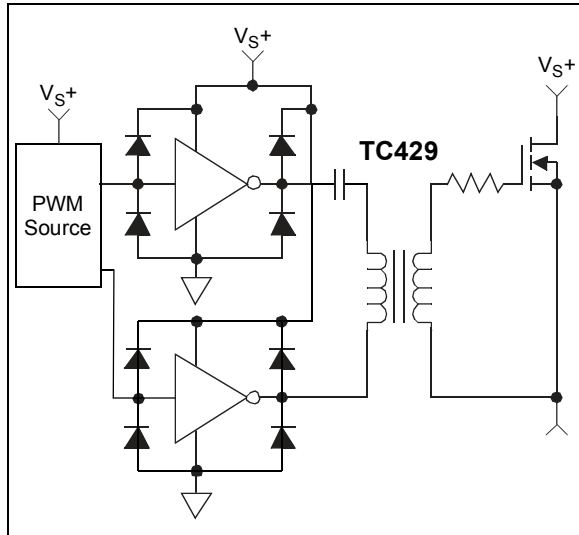


FIGURE 10: TC429's Driving Pulse Transformer.

Germanium diodes, such as a 1N270, will work well also, but may be too leaky for some applications. Standard signal diodes, the 1N4148 or 1N914, for example, are frequently used. Their larger junctions having a lower effective forward drop than the parasitic junctions in the IC work effectively as over/under voltage clamps.

In some instances where standard junction diodes are too leaky (such as might be the case in Figure 10), a very low leakage junction FET (JFET) acting as a diode will do the trick. These devices can have leakage as low as a few picoamps and are very quick in responding. For these applications, contact Microchip Technology Inc.

RESISTORS

In applications where triggering of the parasitic SCR is not a concern and protecting the IC from destruction is the only issue, adding a resistor in series with the power supply pin will prevent device destruction. Once the SCR has been triggered, the supply voltage will have to be brought momentarily to zero to reset the SCR, but no damage will have been done to the IC unless the series resistor was not large enough to limit the fault current to a safe value. This is the lowest cost solution to prevent device damage.

Using the resistor has limitations, however. The resistor will limit the current allowed for the decoupling capacitor, which limits the frequency that the circuit can be driven at due to the $R \times C$ value.

This method works very well in DC op amp circuits, as op-amps draw very little peak current and the circuit is only amplifying DC; no AC component – no $R \times C$ problems.

CONCLUSION

Latch-up in CMOS ICs is preventable. Simple circuit techniques and attention to system design details will ensure that the CMOS' full potential can be realized in all operating environments. Designers can also look forward to the day, in the not too distant future, when even these few simple precautions will no longer be necessary.

Synopsis

To prevent latch-up:

1. Properly decouple IC.
2. Clamp outputs with diodes when driving inductive loads.
3. Clamp inputs with diodes if input signal exceeds the negative or positive rails of the power supply.
4. Use star grounds, if at all possible, in high-current applications.

Note the following details of the code protection feature on Microchip devices:

- Microchip products meet the specification contained in their particular Microchip Data Sheet.
- Microchip believes that its family of products is one of the most secure families of its kind on the market today, when used in the intended manner and under normal conditions.
- There are dishonest and possibly illegal methods used to breach the code protection feature. All of these methods, to our knowledge, require using the Microchip products in a manner outside the operating specifications contained in Microchip's Data Sheets. Most likely, the person doing so is engaged in theft of intellectual property.
- Microchip is willing to work with the customer who is concerned about the integrity of their code.
- Neither Microchip nor any other semiconductor manufacturer can guarantee the security of their code. Code protection does not mean that we are guaranteeing the product as "unbreakable."

Code protection is constantly evolving. We at Microchip are committed to continuously improving the code protection features of our products. Attempts to break microchip's code protection feature may be a violation of the Digital Millennium Copyright Act. If such acts allow unauthorized access to your software or other copyrighted work, you may have a right to sue for relief under that Act.

Information contained in this publication regarding device applications and the like is intended through suggestion only and may be superseded by updates. It is your responsibility to ensure that your application meets with your specifications. No representation or warranty is given and no liability is assumed by Microchip Technology Incorporated with respect to the accuracy or use of such information, or infringement of patents or other intellectual property rights arising from such use or otherwise. Use of Microchip's products as critical components in life support systems is not authorized except with express written approval by Microchip. No licenses are conveyed, implicitly or otherwise, under any intellectual property rights.

Trademarks

The Microchip name and logo, the Microchip logo, KEELOQ, MPLAB, PIC, PICmicro, PICSTART, PRO MATE and PowerSmart are registered trademarks of Microchip Technology Incorporated in the U.S.A. and other countries.


FilterLab, microID, MXDEV, MXLAB, PICMASTER, SEEVAL and The Embedded Control Solutions Company are registered trademarks of Microchip Technology Incorporated in the U.S.A.


Accuron, dsPIC, dsPICDEM.net, ECONOMONITOR, FanSense, FlexROM, fuzzyLAB, In-Circuit Serial Programming, ICSP, ICEPIC, microPort, Migratable Memory, MPASM, MPLIB, MPLINK, MPSIM, PICC, PICKit, PICDEM, PICDEM.net, PowerCal, PowerInfo, PowerTool, rPIC, Select Mode, SmartSensor, SmartShunt, SmartTel and Total Endurance are trademarks of Microchip Technology Incorporated in the U.S.A. and other countries.

Serialized Quick Turn Programming (SQTP) is a service mark of Microchip Technology Incorporated in the U.S.A.

All other trademarks mentioned herein are property of their respective companies.

© 2003, Microchip Technology Incorporated, Printed in the U.S.A., All Rights Reserved.

 Printed on recycled paper.

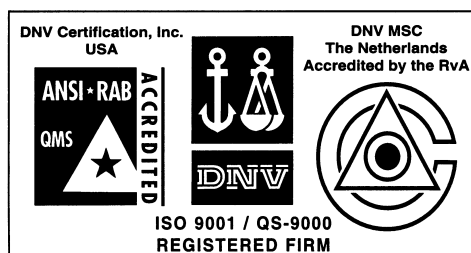

Microchip received QS-9000 quality system certification for its worldwide headquarters, design and wafer fabrication facilities in Chandler and Tempe, Arizona in July 1999 and Mountain View, California in March 2002. The Company's quality system processes and procedures are QS-9000 compliant for its PICmicro® 8-bit MCUs, KEELOQ® code hopping devices, Serial EEPROMs, microperipherals, non-volatile memory and analog products. In addition, Microchip's quality system for the design and manufacture of development systems is ISO 9001 certified.



MICROCHIP

WORLDWIDE SALES AND SERVICE

AMERICAS

Corporate Office

2355 West Chandler Blvd.
Chandler, AZ 85224-6199
Tel: 480-792-7200 Fax: 480-792-7277
Technical Support: 480-792-7627
Web Address: <http://www.microchip.com>

Rocky Mountain

2355 West Chandler Blvd.
Chandler, AZ 85224-6199
Tel: 480-792-7966 Fax: 480-792-4338

Atlanta

3780 Mansell Road, Suite 130
Alpharetta, GA 30022
Tel: 770-640-0034 Fax: 770-640-0307

Boston

2 Lan Drive, Suite 120
Westford, MA 01886
Tel: 978-692-3848 Fax: 978-692-3821

Chicago

333 Pierce Road, Suite 180
Itasca, IL 60143
Tel: 630-285-0071 Fax: 630-285-0075

Dallas

4570 Westgrove Drive, Suite 160
Addison, TX 75001
Tel: 972-818-7423 Fax: 972-818-2924

Detroit

Tri-Atria Office Building
32255 Northwestern Highway, Suite 190
Farmington Hills, MI 48334
Tel: 248-538-2250 Fax: 248-538-2260

Kokomo

2767 S. Albright Road
Kokomo, Indiana 46902
Tel: 765-864-8360 Fax: 765-864-8387

Los Angeles

18201 Von Karman, Suite 1090
Irvine, CA 92612
Tel: 949-263-1888 Fax: 949-263-1338

San Jose

Microchip Technology Inc.
2107 North First Street, Suite 590
San Jose, CA 95131
Tel: 408-436-7950 Fax: 408-436-7955

Toronto

6285 Northam Drive, Suite 108
Mississauga, Ontario L4V 1X5, Canada
Tel: 905-673-0699 Fax: 905-673-6509

ASIA/PACIFIC

Australia

Microchip Technology Australia Pty Ltd
Suite 22, 41 Rawson Street
Epping 2121, NSW
Australia
Tel: 61-2-9868-6733 Fax: 61-2-9868-6755

China - Beijing

Microchip Technology Consulting (Shanghai)
Co., Ltd., Beijing Liaison Office
Unit 915
Bei Hai Wan Tai Bldg.
No. 6 Chaoyangmen Beidajie
Beijing, 100027, No. China
Tel: 86-10-85282100 Fax: 86-10-85282104

China - Chengdu

Microchip Technology Consulting (Shanghai)
Co., Ltd., Chengdu Liaison Office
Rm. 2401-2402, 24th Floor,
Ming Xing Financial Tower
No. 88 TIDU Street
Chengdu 610016, China
Tel: 86-28-86766200 Fax: 86-28-86766599

China - Fuzhou

Microchip Technology Consulting (Shanghai)
Co., Ltd., Fuzhou Liaison Office
Unit 28F, World Trade Plaza
No. 71 Wusi Road
Fuzhou 350001, China
Tel: 86-591-7503506 Fax: 86-591-7503521

China - Hong Kong SAR

Microchip Technology Hongkong Ltd.
Unit 901-6, Tower 2, Metroplaza
223 Hing Fong Road
Kwai Fong, N.T., Hong Kong
Tel: 852-2401-1200 Fax: 852-2401-3431

China - Shanghai

Microchip Technology Consulting (Shanghai)
Co., Ltd.
Room 701, Bldg. B
Far East International Plaza
No. 317 Xian Xia Road
Shanghai, 200051
Tel: 86-21-6275-5700 Fax: 86-21-6275-5060

China - Shenzhen

Microchip Technology Consulting (Shanghai)
Co., Ltd., Shenzhen Liaison Office
Rm. 1812, 18/F, Building A, United Plaza
No. 5022 Binhe Road, Futian District
Shenzhen 518033, China
Tel: 86-755-82901380 Fax: 86-755-82966626

China - Qingdao

Rm. B503, Fullhope Plaza,
No. 12 Hong Kong Central Rd.
Qingdao 266071, China
Tel: 86-532-5027355 Fax: 86-532-5027205

India

Microchip Technology Inc.
India Liaison Office
Divyasree Chambers
1 Floor, Wing A (A3/A4)
No. 11, O'Shaughnessey Road
Bangalore, 560 025, India
Tel: 91-80-2290061 Fax: 91-80-2290062

Japan

Microchip Technology Japan K.K.
Benex S-1 6F
3-18-20, Shinyokohama
Kohoku-Ku, Yokohama-shi
Kanagawa, 222-0033, Japan
Tel: 81-45-471-6166 Fax: 81-45-471-6122

Korea

Microchip Technology Korea
168-1, Youngbo Bldg. 3 Floor
Samsung-Dong, Kangnam-Ku
Seoul, Korea 135-882
Tel: 82-2-554-7200 Fax: 82-2-558-5934

Singapore

Microchip Technology Singapore Pte Ltd.
200 Middle Road
#07-02 Prime Centre
Singapore, 188980
Tel: 65-6334-8870 Fax: 65-6334-8850

Taiwan

Microchip Technology (Barbados) Inc.,
Taiwan Branch
11F-3, No. 207
Tung Hua North Road
Taipei, 105, Taiwan
Tel: 886-2-2717-7175 Fax: 886-2-2545-0139

EUROPE

Austria

Microchip Technology Austria GmbH
Durisolstrasse 2
A-4600 Wels
Austria
Tel: 43-7242-2244-399
Fax: 43-7242-2244-393

Denmark

Microchip Technology Nordic ApS
Regus Business Centre
Lautrup høj 1-3
Ballerup DK-2750 Denmark
Tel: 45 4420 9895 Fax: 45 4420 9910

France

Microchip Technology SARL
Parc d'Activite du Moulin de Massy
43 Rue du Saule Trapu
Batiment A - 1er Etage
91300 Massy, France
Tel: 33-1-69-53-63-20 Fax: 33-1-69-30-90-79

Germany

Microchip Technology GmbH
Steinheilstrasse 10
D-85737 Ismaning, Germany
Tel: 49-89-627-144 0 Fax: 49-89-627-144-44

Italy

Microchip Technology SRL
Centro Direzionale Colleoni
Palazzo Taurus 1 V. Le Colleoni 1
20041 Agrate Brianza
Milan, Italy
Tel: 39-039-65791-1 Fax: 39-039-6899883

United Kingdom

Microchip Ltd.
505 Eskdale Road
Winnesh Triangle
Wokingham
Berkshire, England RG41 5TU
Tel: 44 118 921 5869 Fax: 44-118 921-5820

12/05/02