

Wattmeter reading:

$$P_1 = k_w \alpha_w \quad k_w = \frac{r_V \cdot r_A}{d} \cos \varphi_w$$

Wattmeter and voltmeter consumption:

$$P'_W = \frac{U_{L1}^2}{R_W} \quad P'_V = \frac{U_{L1L2}^2}{R_V} \quad U_{L1} = \frac{U_{L1L2}}{\sqrt{3}}$$

Three phase input power:

$$P_3 = 3 (P_1 - P'_W - P'_V) = 3 P_{L1}$$

Power factor:

$$\cos \varphi = \frac{P_{L1}}{U_{L1} I_{L1}}$$


2. POWER MEASUREMENT for Unbalanced FOUR-WIRE, WYE-Connected Load (the neutral conductor, with).

Task:

Having been realized, the 3 – PHASE-WYE connected LOAD (the three various resistors); by the electronic wattmeter using, to measure:

- either the **average power in each phase**;
- and either the **total average power**, too.

Diagram:

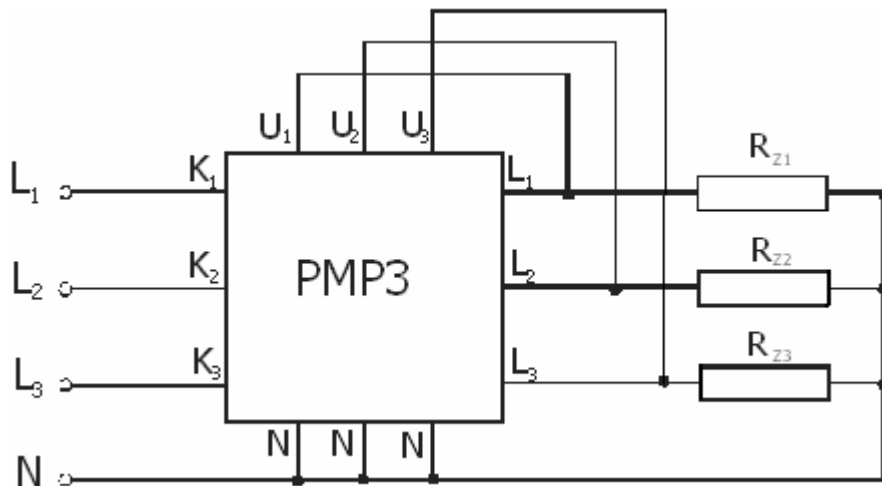

Instruments:

PMP3 ... the electronic programmable ELKO ŠŤOVÍČEK

R_{Z1} ... load resistor 250 Ω (lab 57 ... 400 Ω)

R_{Z2} ... load resistor 450 Ω (lab 57 ... 600 Ω)

R_{Z3} ... load resistor 600 Ω (lab 57 ... 1200 Ω)

Measured and computed values:

V _{L1} [V]	I _{L1} [A]	P _{L1} [W]	V _{L2} [V]	I _{L2} [A]	P _{L2} [W]	V _{L3} [V]	I _{L2} [A]	P _{L3} [W]	P ₃ [W]	cos φ [-]

Note:

The electronic wattmeter has to be controlled in agreement the enclosed instructions, with.

3. TWO WATTMETER METHOD (Aron's Method)

- for the **TOTAL POWER MEASUREMENT** in a **THREE-PHASE** system (no-neutral conductor, with).

Task:

Two Wattmeter Method - being applied to the THREE resistors DELTA -connected LOAD; to measure the **input power**.

To compute – being respected – the instruments consumptions.

Instruments:

V_{AC} ...ferromagnetic voltmeter 500V

R_{Z1} ... load resistor 410 Ω


A_{AC} ...ferromagnetic ammeter 2A

R_{Z2} ... load resistor 600 Ω

W ... ferrodynamic wattmeter 360V/2A

R_{Z3} ... load resistor 1200 Ω

Diagram:

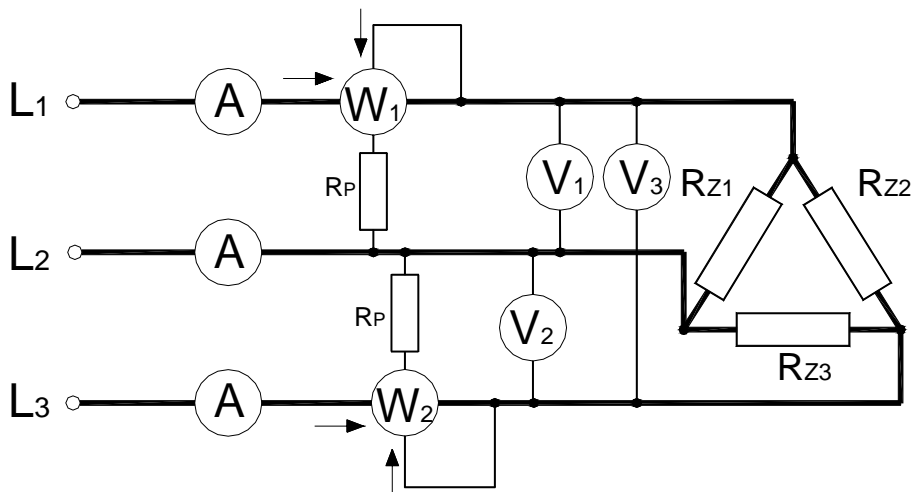

Measured and computed values:

V_{L1L2} [V]	I_{L1} [A]	α_{W1} [d]	k_{W1} [W/d]	V_{L2L3} [V]	I_{L3} [A]	α_{W2} [d]	k_{W2} [W/d]	I_2 [A]	V_{L1L3} [V]	R_w [Ω]	R_v [Ω]	P' [W]	P_3 [W]

Calculation:

wattmeter consumption; and voltmeter consumption:

$$P'_{W1} = \frac{U_{L1L2}^2}{(R_{W1} + R_p)} \quad P'_{W2} = \frac{U_{L2L3}^2}{(R_{W2} + R_p)} \quad P'_{V1} = \frac{U_{L1L2}^2}{R_{V1}} \quad P'_{V2} = \frac{U_{L2L3}^2}{R_{V2}}$$

3 - phase input power:


$$P_3 = |k_{W1} \alpha_{W1} + k_{W2} \alpha_{W2}| - P' \quad P' = P'_{W1} + P'_{W2} + P'_{V1} + P'_{V2}$$

4. REACTIVE POWER MEASUREMENT in a THREE-PHASE system

Task: To measure the **reactive input power** Q of asynchronous motor by no-load test – using **ONE – Wattmeter Method**.

To sketch the phasor diagram – the measured voltages, for.

Diagram:

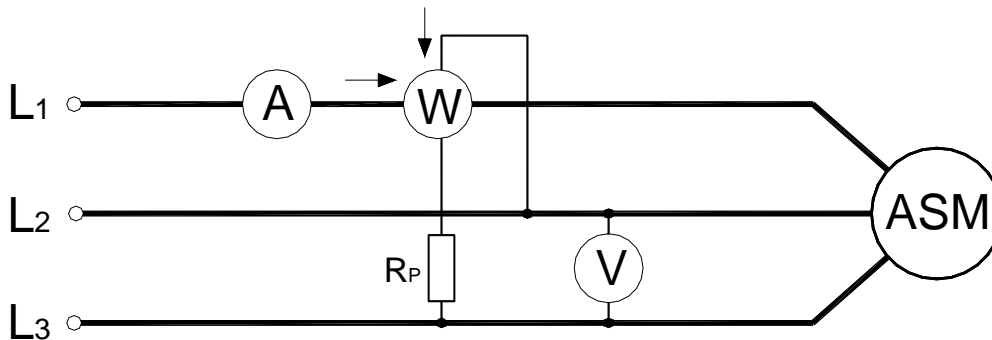

Note:

To be measured the reactive power (by the average power wattmeter using) – the voltage coil has to be connected the voltage **lags 90°**, on – with respect to the corresponding voltage.

These one voltage is the line – to line voltage:

- (between line L2 and L3), if it's measured in line L1;
- (between L3 and L1), if measured in L2;
- (between L1 and L2), if measured in L3;

Instruments:

V_{AC} ...ferromagnetic voltmeter 500V

W ... ferrodynamic wattmeter 360V/2A

A_{AC} ...ferromagnetic ammeter 2A

Measured and computed values:

α_{w1} [d]	k_{w1} [VAr/d]	α_{w2} [d]	k_{w2} [VAr/d]	α_{w3} [d]	k_{w3} [VAr/d]	Q [VAr]

Calculation:

$$Q = \frac{1}{\sqrt{3}} (k_{w1} \alpha_{w1} + k_{w2} \alpha_{w2} + k_{w3} \alpha_{w3})$$

Simplification – for the **one – phase** measurement, only:.

$$Q = 3 \frac{1}{\sqrt{3}} (k_{w1} \alpha_{w1})$$