

Chapter # 4: Programmable and Steering Logic

Contemporary Logic Design

Randy H. Katz
University of California, Berkeley


June 1993

No. 4-1

PALs and PLAs

Pre-fabricated building block of many AND/OR gates (or NOR, NAND) "Personalized" by making or breaking connections among the gates

Programmable Array Block Diagram for Sum of Products Form

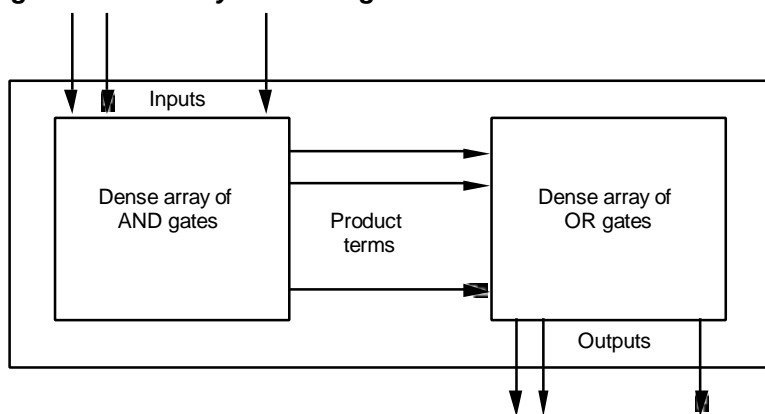

No. 4-2

Key to Success: Shared Product Terms

Example: $F_0 = A + B' C'$
 $F_1 = A C' + A B$
 $F_2 = B' C' + A B$
 $F_3 = B' C + A$

Personality Matrix

Product term	Inputs			Outputs			
	A	B	C	F ₀	F ₁	F ₂	F ₃
AB	1	1	-	0	1	1	0
\overline{BC}	-	0	1	0	0	0	1
\overline{AC}	1	-	0	0	1	0	0
\overline{BC}	-	0	0	1	0	1	0
A	1	-	-	1	0	0	1

Reuse of terms

Input Side:

1 = asserted in term
 0 = negated in term
 - = does not participate

Output Side:


1 = term connected to output
 0 = no connection to output

No. 4-3

Example Continued


All possible connections are available before programming

Figure 3.13a. PAL before programming

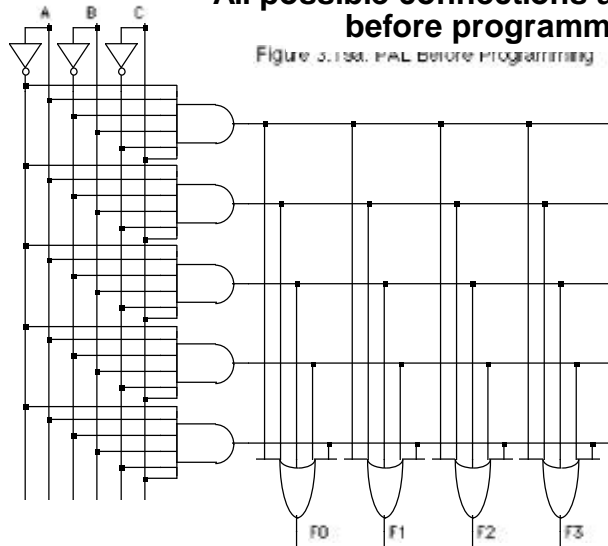

No. 4-4


Example Continued

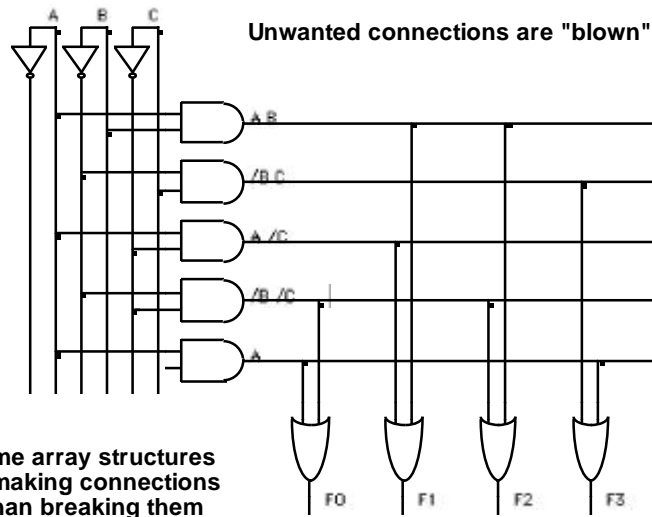


Note: some array structures work by making connections rather than breaking them

No. 4-5

 Alternative representation for high fan-in structures



 Short-hand notation so we don't have to draw all the wires!



Notation for implementing

$$F0 = A B + A' B'$$

$$F1 = C D' + C' D$$

No. 4-6

Design Example

Multiple functions of A, B, C

$$F1 = A B C$$


$$F2 = A + B + C$$

$$F3 = \overline{A B C}$$

$$F4 = \overline{A + B + C}$$


$$F5 = A \text{ xor } B \text{ xor } C$$
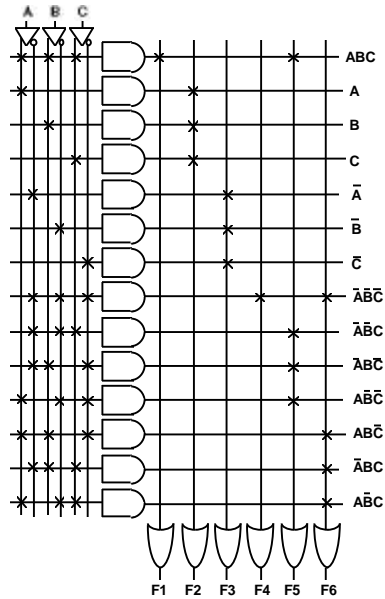
$$F6 = A \text{ xnor } B \text{ xnor } C$$



What is difference between Programmable Array Logic (PAL) and Programmable Logic Array (PLA)?

 PAL concept — implemented by Monolithic Memories
constrained topology of the OR Array







**A given column of the OR array
has access to only a subset of
the possible product terms**

PLA concept — generalized topologies in AND and OR planes

Design Example: BCD to Gray Code Converter

A	B	C	D	W	X	Y	Z
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	1
0	0	1	1	0	0	1	0
0	1	0	0	0	1	1	0
0	1	0	1	1	1	1	0
0	1	1	0	1	0	1	0
0	1	1	1	1	0	1	1
1	0	0	0	1	0	0	1
1	0	0	1	1	0	0	0
1	0	1	0	X	X	X	X
1	0	1	1	X	X	X	X
1	1	0	0	X	X	X	X
1	1	0	1	X	X	X	X
1	1	1	0	X	X	X	X
1	1	1	1	X	X	X	X

    

$$W = A + B D + B C$$


$$X = B C'$$

$$Y = B + C$$

$$Z = A'B'C'D + B C D + A D' + B' C D'$$

No. 4-9


Programmed PAL:

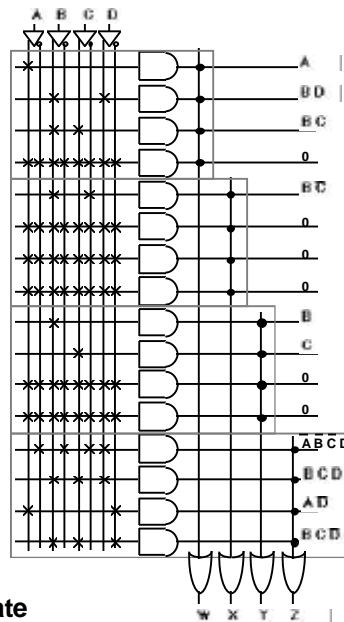

4 product terms per each OR gate

No. 4-10

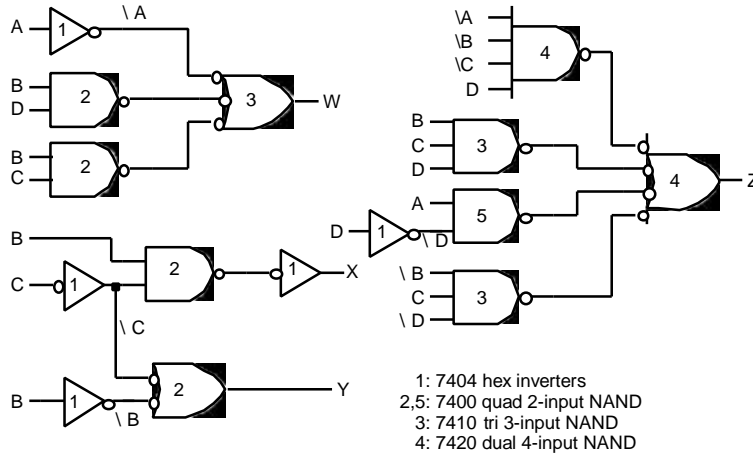
Code Converter Discrete Gate Implementation



4 SSI Packages vs. 1 PL/PAL Package!

No. 4-11

Another Example: Magnitude Comparator

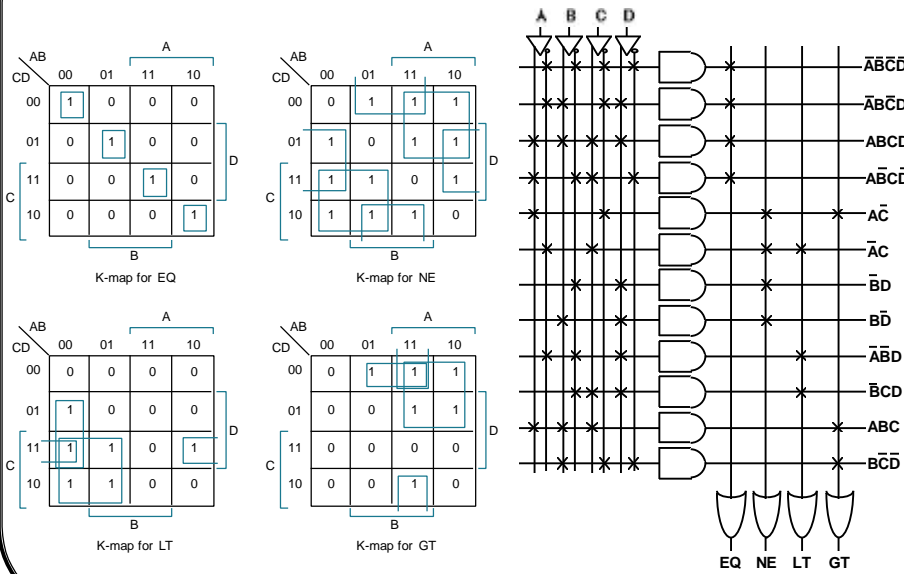

No. 4-12

Non-Gate Logic

Introduction

AND-OR-Invert
PAL/PLA

Generalized Building Blocks
Beyond Simple Gates

Kinds of "Non-gate logic":


- switching circuits built from CMOS transmission gates
- multiplexer/selecter functions
- decoders
- tri-state and open collector gates
- read-only memories

No. 4-13

Selection Function/Demultiplexer Function with Transmission Gates


Selector:

 Choose I_0 if $S = 0$
Choose I_1 if $S = 1$



Demultiplexer:


I to Z_0 if $S = 0$
 I to Z_1 if $S = 1$

 

No. 4-14

Well-formed Switching Networks

 Problem with the Demux implementation:
multiple outputs, but only one connected to the input!




The fix: additional logic to drive every output to a known value
Never allow outputs to "float"

No. 4-15

Multiplexers/Selectors

Multi-point connections

 

Multiple input sources

Multiple output destinations

No. 4-16

General Concept

2^n data inputs, n control inputs, 1 output


used to connect 2^n points to a single point

control signal pattern form binary index of input connected to output


$$Z = A' I_0 + A I_1$$

Functional form


Logical form

 

 
**Two alternative forms
for a 2:1 Mux Truth Table**



$$Z = A' I_0 + A I_1$$

 
 
$$Z = A' B' I_0 + A' B I_1 + A B' I_2 + A B I_3$$




$$Z = A' B' C' I_0 + A' B' C I_1 + A' B C' I_2 + A' B C I_3 + A B' C' I_4 + A B' C I_5 + A B C' I_6 + A B C I_7$$

In general, $Z = \sum_{k=0}^{2^n-1} m_k I_k$


in minterm shorthand form for a $2^n : 1$ Mux

Alternative Implementations

 

Gate Level Implementation of 4:1 Mux

thirty six transistors

 


Transmission Gate Implementation of 4:1 Mux

twenty transistors

No. 4-19


Large multiplexers can be implemented by cascaded smaller ones

 

Alternative 8:1 Mux Implementation

Control signals B and C simultaneously choose one of I_0 - I_3 and I_4 - I_7

Control signal A chooses which of the upper or lower MUX's output to gate to Z

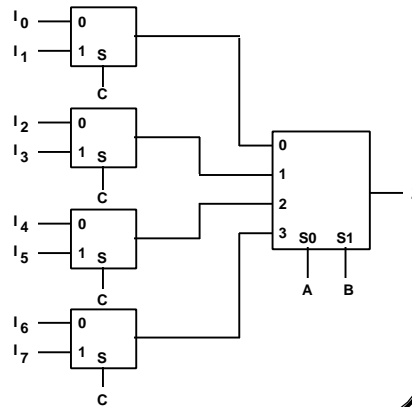

No. 4-20

Multiplexers/selectors as a general purpose logic block

2^{n-1} :1 multiplexer can implement any function of n variables


n-1 control variables; remaining variable is a data input to the mux

Example:


$$F(A,B,C) = m_0 + m_2 + m_6 + m_7$$

$$= A' B' C' + A' B C' + A B C' + A B C$$
 
$$= A' B' (C') + A' B (C') + A B' (0) + A B (1)$$




A	B	C	F
0	0	0	1 \overline{C}
0	0	1	0 \overline{C}
0	1	0	1 \overline{C}
0	1	1	0 \overline{C}
1	0	0	0 0
1	0	1	0 0
1	1	0	1 1
1	1	1	1 1

 

"Lookup Table"

No. 4-21

Generalization

 


Four possible configurations of the truth table rows

Can be expressed as a function of $I_n, 0, 1$

No. 4-22

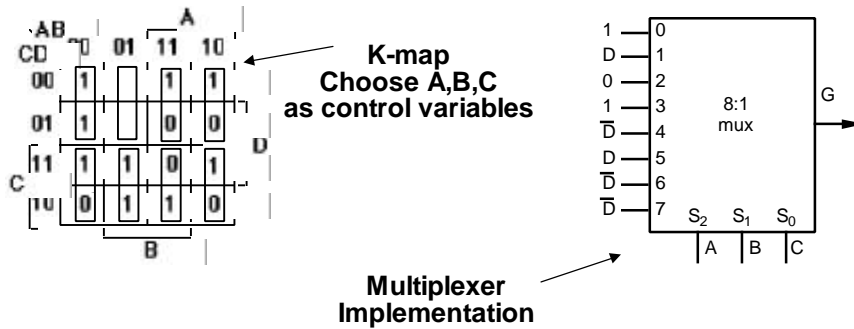Example:

G(A,B,C,D) can be implemented by an 8:1 MUX:



TTL package efficient
May be gate inefficient

Decoders/Demultiplexers

Decoder: single data input, n control inputs, 2^n outputs

- control inputs (called **select S**) represent Binary index of output to which the input is connected
- data input usually called "**enable**" (**G**)

1:2 Decoder:

$$O0 = G \cdot \overline{S}; \quad O1 = G \cdot S$$

2:4 Decoder:

$$O0 = G \cdot \overline{S0} \cdot \overline{S1}$$

$$O1 = G \cdot \overline{S0} \cdot S1$$

$$O2 = G \cdot S0 \cdot \overline{S1}$$

$$O3 = G \cdot S0 \cdot S1$$

3:8 Decoder:

$$O0 = G \cdot \overline{S0} \cdot \overline{S1} \cdot \overline{S2}$$

$$O1 = G \cdot \overline{S0} \cdot \overline{S1} \cdot S2$$

$$O2 = G \cdot \overline{S0} \cdot S1 \cdot \overline{S2}$$

$$O3 = G \cdot \overline{S0} \cdot S1 \cdot S2$$


$$O4 = G \cdot S0 \cdot \overline{S1} \cdot \overline{S2}$$

$$O5 = G \cdot S0 \cdot \overline{S1} \cdot S2$$


$$O6 = G \cdot S0 \cdot S1 \cdot \overline{S2}$$

$$O7 = G \cdot S0 \cdot S1 \cdot S2$$


Alternative Implementations

 


1:2 Decoder, Active High Enable

 

1:2 Decoder, Active Low Enable

 


2:4 Decoder, Active High Enable

 


2:4 Decoder, Active Low Enable

No. 4-25

Switch Logic Implementations

 


Naive, Incorrect Implementation
All outputs not driven at all times

 

Correct 1:2 Decoder Implementation

No. 4-26

Switch Implementation of 2:4 Decoder

 

Operation of 2:4 Decoder


$S_0 = 0, S_1 = 0$

one straight thru path

three diagonal paths

No. 4-27

Decoder as a Logic Building Block

 

Decoder Generates Appropriate Minterm based on Control Signals

Example Function:

$$F_1 = A' B C' D + A' B' C D + A B C D$$


$$F_2 = A B C' D' + A B C$$

$$F_3 = (A' + B' + C' + D')$$

No. 4-28

Decoder/Demultiplexer

Decoder as a Logic Building Block

 


If active low enable, then use NAND gates!


No. 4-29

Multiplexers/Decoders

Alternative Implementations of 32:1 Mux

 

Multiplexer Only

 


Multiplexer + Decoder

No. 4-30

Multiplexers/Decoders

5:32 Decoder

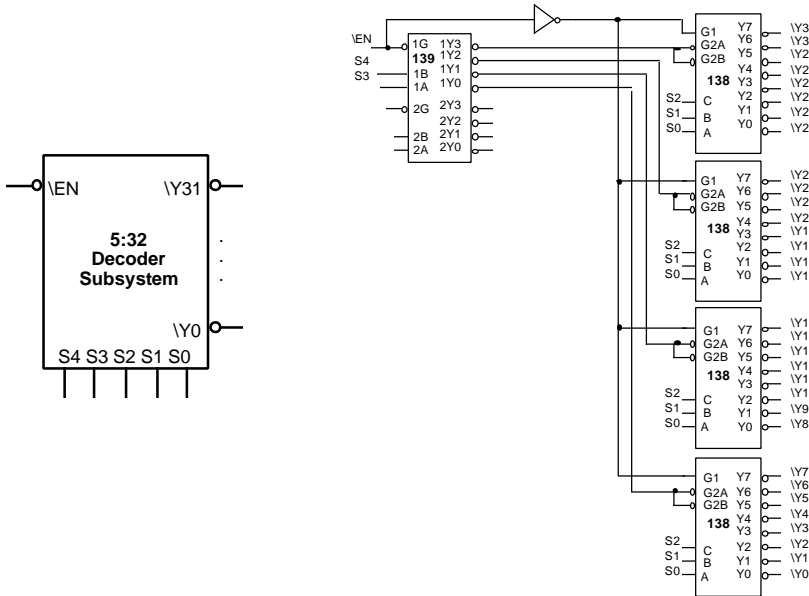

No. 4-31

Tri-State and Open-Collector

The Third State

Logic States: "0", "1"

Don't Care/Don't Know State: "X" (must be some value in real circuit!)

Third State: "Z" — high impedance — infinite resistance, no connection

Tri-state gates: output values are "0", "1", and "Z"
 additional input: output enable (OE)


A	OE	F
X	0	Z
0	1	0
1	1	1

When OE is high, this gate is a non-inverting "buffer"

When OE is low, it is as though the gate was *disconnected* from the output!

This allows more than one gate to be connected to the same output wire, as long as only one has its output enabled *at the same time*


Non-inverting buffer's timing waveform

 

No. 4-32

Tri-state and Open Collector

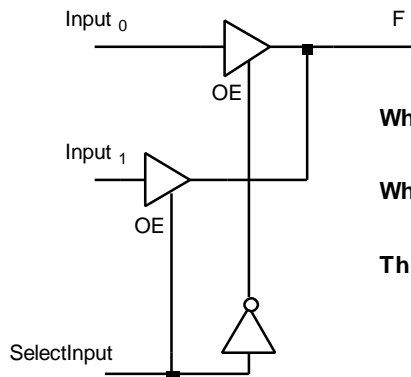Using tri-state gates to implement an economical multiplexer:



When SelectInput is asserted high
Input₁ is connected to F


When SelectInput is driven low
Input₀ is connected to F

This is essentially a 2:1 Mux


No. 4-33

Tri-state and Open Collector

Alternative Tri-state Fragment

 

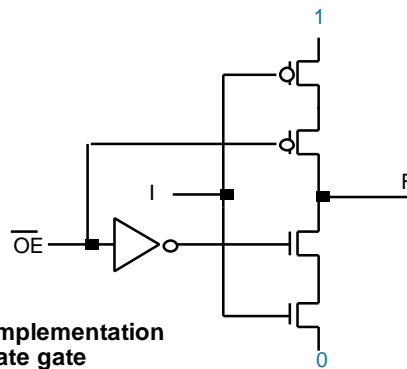Active low tri-state enables
plus inverting tri-state buffers




Switch Level Implementation
of tri-state gate

No. 4-34

Tri-State and Open Collector

4:1 Multiplexer, Revisited

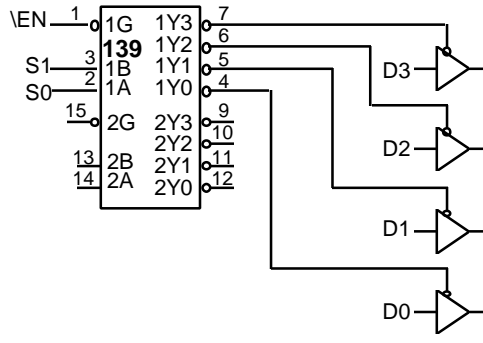

Decoder + 4 tri-state Gates

No. 4-35


Tri-State and Open Collector

Open Collector

another way to connect multiple gates to the same output wire

gate only has the ability to pull its output low; it cannot actively drive the wire high

 this is done by pulling the wire up to a logic 1 voltage through a resistor




OC NAND gates

Wired AND:

If A and B are "1", output is actively pulled low
if C and D are "1", output is actively pulled low
if one gate is low, the other high, then low wins
if both gates are "1", the output floats, pulled high by resistor


Hence, the two NAND functions are AND'd together!

 

No. 4-36

Tri-State and Open Collector

4:1 Multiplexer

 

Decoder + 4 Open Collector Gates

No. 4-37


Read-Only Memories

ROM: Two dimensional array of 1's and 0's

Row is called a "word"; index is called an "address"

Width of row is called *bit-width* or *wordsize*

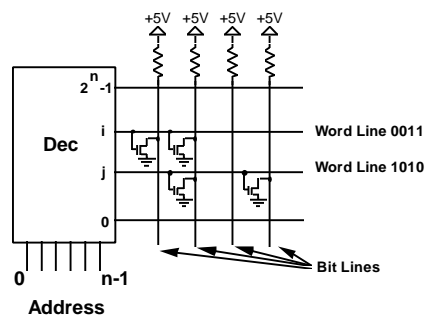Address is input, selected word is output



Internal Organization

No. 4-38

Read-Only Memories


Example: Combination Logic Implementation

$$F_0 = A' B' C + A B' C' + A B' C$$

$$F_1 = A' B' C + A' B C' + A B C$$

$$F_2 = A' B' C' + A' B' C + A B' C'$$


$$F_3 = A' B C + A B' C' + A B C'$$

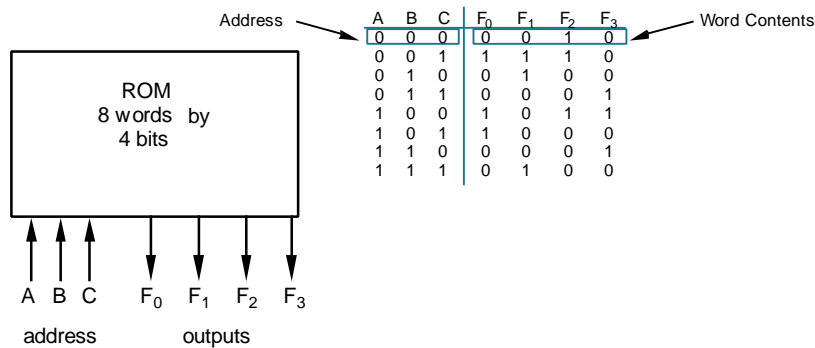

No. 4-39

Read-Only Memories

 Not unlike a PLA structure with a fully decoded AND array!



ROM vs. PLA:

ROM approach advantageous when

- (1) design time is short (no need to minimize output functions)
- (2) most input combinations are needed (e.g., code converters)
- (3) little sharing of product terms among output functions

ROM problem: size doubles for each additional input, can't use don't cares

PLA approach advantageous when



- (1) design tool like espresso is available
- (2) there are relatively few unique minterm combinations
- (3) many minterms are shared among the output functions

PAL problem: constrained fan-ins on OR planes

No. 4-40

Read-Only Memories

2764 EPROM
8K x 8

  

16K x 16
Subsystem

No. 4-41

Combinational Logic Word Problems

General Design Procedure

1. Understand the Problem
what is the circuit supposed to do?
write down inputs (data, control) and outputs
draw block diagram or other picture
2. Formulate the Problem in terms of a truth table or other suitable design representation
truth table or waveform diagram
3. Choose Implementation Target
ROM, PAL, PLA, Mux, Decoder + OR, Discrete Gates
4. Follow Implementation Procedure
K-maps, espresso, misII

No. 4-42

Combinational Logic Word Problems

Process Line Control Problem

Statement of the Problem

Rods of varying length (+/-10%) travel on conveyor belt
Mechanical arm pushes rods within spec (+/-5%) to one side
Second arm pushes rods too long to other side
Rods too short stay on belt

3 light barriers (light source + photocell) as sensors

Design combinational logic to activate the arms

Understanding the Problem

Inputs are three sensors, outputs are two arm control signals

Assume sensor reads "1" when tripped, "0" otherwise


Call sensors A, B, C

Draw a picture!

No. 4-43

Combinational Logic Word Problems

Process Control Problem

 


Where to place the light sensors A, B, and C to distinguish among the three cases?

Assume that A detects the leading edge of the rod on the conveyor

No. 4-44

Combinational Logic Word Problems

Process Control Problem

 

A to B distance place apart at specification - 5%

A to C distance placed apart at specification +5%

No. 4-45

Combinational Logic Word Problems

Process Control Problem

A	B	C	Function
0	0	0	X
0	0	1	X
0	1	0	X
0	1	1	X
1	0	0	too short
1	0	1	X
1	1	0	in spec
1	1	1	too long

Truth table and logic implementation now straightforward

"too long" = $A B C$
(all three sensors tripped)

"in spec" = $A B C'$
(first two sensors tripped)

No. 4-46

Combinational Logic Word Problems

BCD to 7 Segment Display Controller



Understanding the problem:

input is a 4 bit bcd digit

output is the control signals for the display

4 inputs A, B, C, D

7 outputs C0 — C6

  

Block Diagram

No. 4-47

Combinational Logic Word Problems

BCD to 7 Segment Display Controller

A	B	C	D	C0	C1	C2	C3	C4	C5	C6
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	1	1	1	1	1	1	0
0	0	1	0	1	1	1	1	1	1	1
0	0	1	1	1	1	1	1	1	1	1
0	1	0	0	1	1	1	1	1	1	1
0	1	0	1	1	1	1	1	1	1	1
0	1	1	0	1	1	1	1	1	1	1
0	1	1	1	1	1	1	1	1	1	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	1	1	1
1	0	1	0	>	>	>	>	>	>	X
1	0	1	1	>	>	>	>	>	>	X
1	1	0	0	>	>	>	>	>	>	X
1	1	0	1	>	>	>	>	>	>	X
1	1	1	0	>	>	>	>	>	>	X
1	1	1	1	>	>	>	>	>	>	X

Formulate the problem in terms of a truth table

Choose implementation target:

if ROM, we are done

don't cares imply PAL/PLA may be attractive

Follow implementation procedure:


hand reduced K-maps

vs.

espresso

No. 4-48

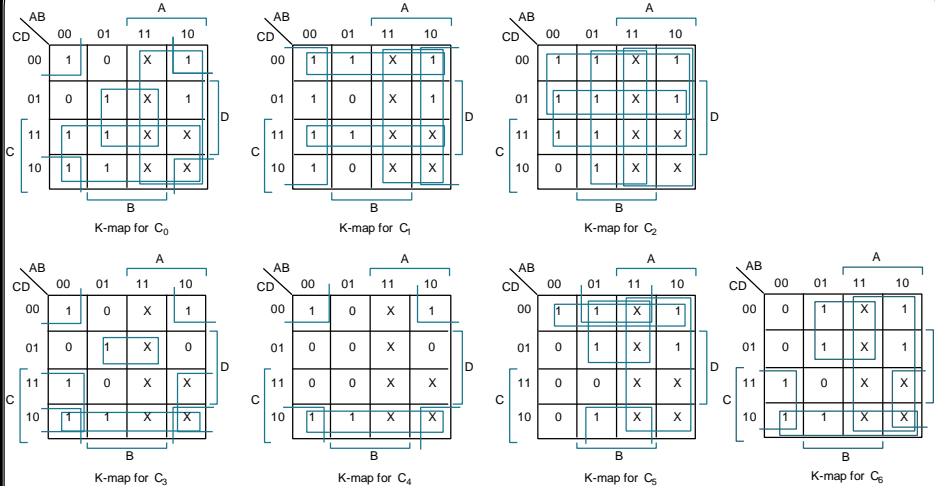Combinational Logic Word Problems
BCD to 7 Segment Display Controller




$$\begin{aligned}
 C0 &= A + B D + C + B' D' & C3 &= B' D' + C D' + B C' D + B' C \\
 C1 &= A + C' D' + C D + B' & C4 &= B' D' + C D \\
 C2 &= A + B + C' + D & C5 &= A + C' D' + B D' + B C' \\
 C6 &= A + C D' + B C' + B' C
 \end{aligned}$$

14 Unique Product Terms

Combinational Logic Word Problems
BCD to 7 Segment Display Controller

16H8PAL
Can Implement
the function

 


Note: Fuse number = first fuse number + increment

Combinational Logic Word Problems

BCD to 7 Segment Display Controller

14H8PAL
Cannot Implement
the function

 


No. 4-51

Combinational Logic Word Problems

BCD to 7 Segment Display Controller

PLA Implementation

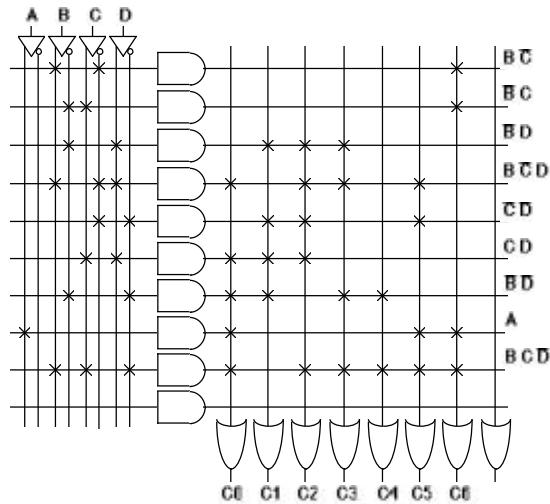

No. 4-52

Combinational Logic Word Problems

BCD to 7 Segment Display Controller

Multilevel Implementation

$$X = C' + D'$$

$$Y = B' C'$$

$$C0 = C3 + A' B X' + A D Y$$

$$C1 = Y + A' C5' + C' D' C6$$

$$C2 = C5 + A' B' D + A' C D$$

$$C3 = C4 + B D C5 + A' B' X'$$

$$C4 = D' Y + A' C D'$$

$$C5 = C' C4 + A Y + A' B X$$

$$C6 = A C4 + C C5 + C4' C5 + A' B' C$$

52 literals

33 gates

Ineffective use of don't cares

No. 4-53

Combinational Logic Word Problems

Logical Function Unit

Statement of the Problem:

C	C	C2	F	Comments
1	1	0	1	always 1
1	1	1	A + B	logical or
1	1	0	A·B	logical nand
1	1	1	A xor B	logical xor
1	1	0	A xnor B	logical xnor
1	1	1	A·B	logical and
1	1	0	A+B	logical nor
1	1	1	0	always 0

3 control inputs: C0, C1, C2

2 data inputs: A, B

1 output: F

No. 4-54


Combinational Logic Word Problems

Logical Function Unit

C	C	C	A	B	F
0	0	0	0	0	0
0	0	0	0	1	0
0	0	0	1	0	0
0	0	0	1	1	0
0	0	1	0	0	0
0	0	1	0	1	0
0	0	1	1	0	0
0	0	1	1	1	0
0	1	0	0	0	0
0	1	0	0	1	0
0	1	0	1	0	0
0	1	0	1	1	0
0	1	1	0	0	0
0	1	1	0	1	0
0	1	1	1	0	0
0	1	1	1	1	0
1	0	0	0	0	0
1	0	0	0	1	0
1	0	0	1	0	0
1	0	0	1	1	0
1	0	1	0	0	0
1	0	1	0	1	0
1	0	1	1	0	0
1	0	1	1	1	0
1	1	0	0	0	0
1	1	0	0	1	0
1	1	0	1	0	0
1	1	0	1	1	0
1	1	1	0	0	0
1	1	1	0	1	0
1	1	1	1	0	0
1	1	1	1	1	0

Formulate as a truth table

 
Choose implementation technology
 5-variable K-map
 espresso
 multiplexor implementation



Combinational Logic Word Problems

Logical Function Unit

Follow implementation procedure


 


$$F = C_2' A' B' + C_0' A B' + C_0' A' B + C_1' A B$$

5 gates, 5 inverters

Also four packages:
 4 x 3-input NAND
 1 x 4-input NAND

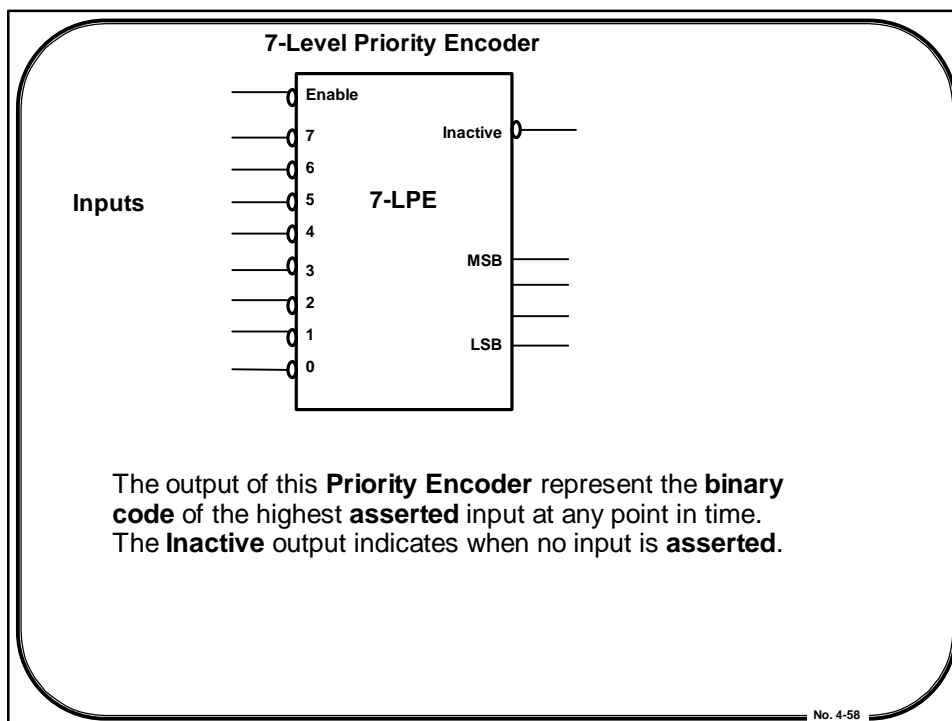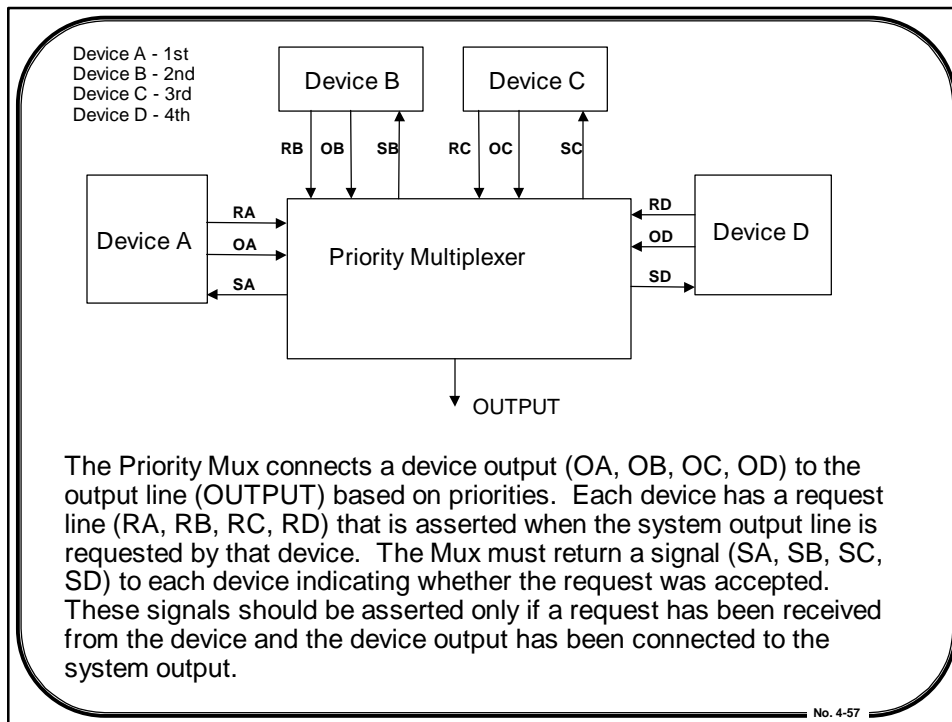Alternative: 32 x 1-bit ROM
 single package



Chapter Review

- ***Non-Simple Gate Logic Building Blocks:***

- PALs/PLAs

- Multiplexers/Selectors

- Decoders

- ROMs

- Tri-state, Open Collector

- ***Combinational Word Problems:***

- Understand the Problem

- Formulate in terms of a Truth Table

- Choose implementation technology

- Implement by following the design procedure