

## Tutorial Outline

8:30 - 8:45	Introduction and motivation
8:45 - 9:05	Sources of power in CMOS designs
9:05 - 9:30	Power analysis tools and techniques
9:30 - 10:30	Gate & functional unit design issues & techniques
10:30 - 10:50	BREAK
10:50 - 12:15	Architectural level issues and techniques
12:15 - 1:30	LUNCH
1:30 - 2:30	Low power memory system design
2:30 - 3:30	Software level issues and techniques
3:30 - 3:50	BREAK
3:50 - 4:30	Software level issues and techniques, con't
4:30 - 4:45	Future challenges

ISCA Tutorial: Low Power Design

Sources.1

©MJl&VN, PSU, 2000

## Where Does Power Go in CMOS?

- **Dynamic Power Consumption**
  - » charging and discharging capacitors
- **Short Circuit Currents**
  - » short circuit path between supply rails during switching
- **Leakage Current**
  - » leaking diodes and transistors
- **Static Currents**
  - » design styles such as pseudo NMOS

ISCA Tutorial: Low Power Design

Sources.2


©MJl&VN, PSU, 2000

## CMOS Gate Energy & Power Equations

$$E = C_L V_{DD}^2 P_{0 \rightarrow 1} + t_{sc} V_{DD} I_{peak} P_{0 \rightarrow 1} + V_{DD} I_{leakage}$$

$$P = C_L V_{DD}^2 f_{0 \rightarrow 1} + t_{sc} V_{DD} I_{peak} f_{0 \rightarrow 1} + V_{DD} I_{leakage}$$

## Dynamic Power Consumption

 

$$\text{Energy/transition} = C_L * V_{DD}^2 * P_{0 \rightarrow 1}$$

$$\text{Power} = \text{Energy/transition} * f = C_L * V_{DD}^2 * P_{0 \rightarrow 1} * f$$

Not a function of transistor sizes!  
Data dependent - a function of **switching activity!**

## Lowering Dynamic Power

- Reducing  $V_{DD}$  has a **quadratic** effect!
  - » Has a negative effect on performance especially as  $V_{DD}$  approaches  $2V_T$
- Lowering  $C_L$ 
  - » Improves performance as well
  - » Keep transistors minimum size (keeps **intrinsic** capacitance (gate and diffusion) small)
  - » Transistors should be sized only when  $C_L$  is dominated by **extrinsic** capacitance (fanout and wires)
- Reducing the switching activity,  $f_{0 \rightarrow 1} = P_{0 \rightarrow 1} * f$ 
  - » A function of signal statistics and clock rate
  - » Impacted by logic and architecture design decisions

ISCA Tutorial: Low Power Design

Sources.5

©MJ&VN, PSU, 2000

## Dynamic Power Consumption is Data Dependent

Static 2-input NOR Gate

A	B	Out
0	0	1
0	1	0
1	0	0
1	1	0

Assume **signal probabilities**

$$P_{A=1} = 1/2$$

$$P_{B=1} = 1/2$$

Then **transition probability**

$$P_{0 \rightarrow 1} = P_{\text{out}=0} \times P_{\text{out}=1}$$


$$= 3/4 \times 1/4 = 3/16$$

ISCA Tutorial: Low Power Design

Sources.6

©MJ&VN, PSU, 2000



## NOR Gate Transition Probabilities

 


$$P_{0 \rightarrow 1} = P_0 \times P_1 = (1 - (1 - P_A)(1 - P_B))(1 - P_A)(1 - P_B)$$

$P_{0 \rightarrow 1}$  is a strong function of signal statistics

## Glitching in Static CMOS Networks

  


## Glitching in an RCA

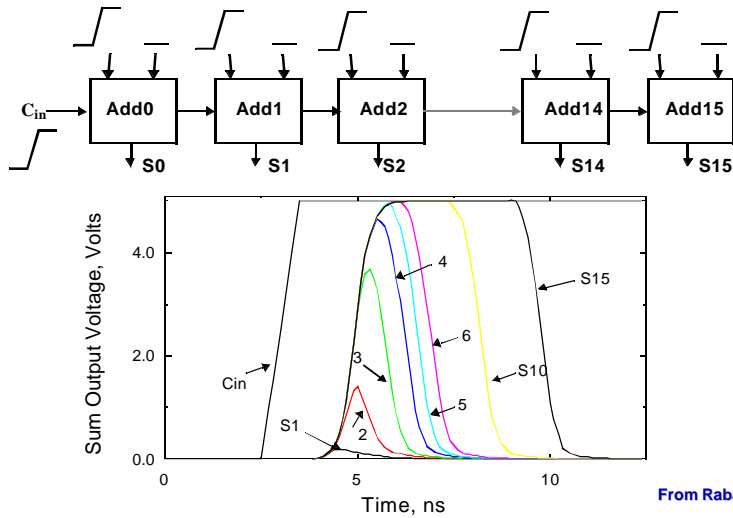

ISCA Tutorial: Low Power Design

Sources.9

## Short Circuit Power Consumption

 

Finite slope of the input signal causes a direct current path between  $V_{DD}$  and GND for a short period of time during switching when both the NMOS and PMOS transistors are conducting.

ISCA Tutorial: Low Power Design

Sources.10

©MJl&VN, PSU, 2000


## Short Circuit Currents Determinates

$$E_{sc} = t_{sc} V_{DD} I_{peak} P_{0 \rightarrow 1}$$

$$P_{sc} = t_{sc} V_{DD} I_{peak} f_{0 \rightarrow 1}$$

- Duration and slope of the input signal,  $t_{sc}$
- $I_{peak}$  determined by
  - » the saturation current of the P and N transistors which depend on their **sizes**, process technology, temperature, etc.
  - » the ratio between input and output slopes – function of  $C_L$

## $I_{sc}$ as a Function of $C_L$

 


500 psec input slope

When load capacitance is small, power is dominated by  $I_{sc}$ .


Short circuit dissipation is minimized by matching the rise/fall times of the input and output signals - **slope engineering**.

# Leakage Power

 

Sub-threshold current is the dominant factor.  
Increases **exponentially** with temperature!

# Sub-Threshold in MOS

 

Continued scaling of supply voltage will make subthreshold conduction a dominate source of power dissipation.

## Basic Principles of Low Power Design

$$P = C_L V_{DD}^2 f_{0 \rightarrow 1} + t_{sc} V_{DD} I_{peak} f_{0 \rightarrow 1} + V_{DD} I_{leakage}$$

- Reduce switching (supply) voltage
  - » quadratic effect -> dramatic savings
  - » negative effect on performance
- Reduce capacitance
- Reduce switching frequency
  - » switching activity
  - » clock rate
- Reduce glitching
- Reduce short circuit currents (slope engineering)
- Reduce leakage currents